




Physics Teacher  
Mahmoud Ismail

## Under the auspices of the Cairo Teachers Syndicate

The Egyptian Gazette newspaper is interested in boosting community participation and offering services to students through providing the strongest educational content in various subjects. This comes according to the latest standards of the Egyptian Ministry of Education and under the supervision of a group of the best teachers.




Educational Consultant  
Awatf Ahmed

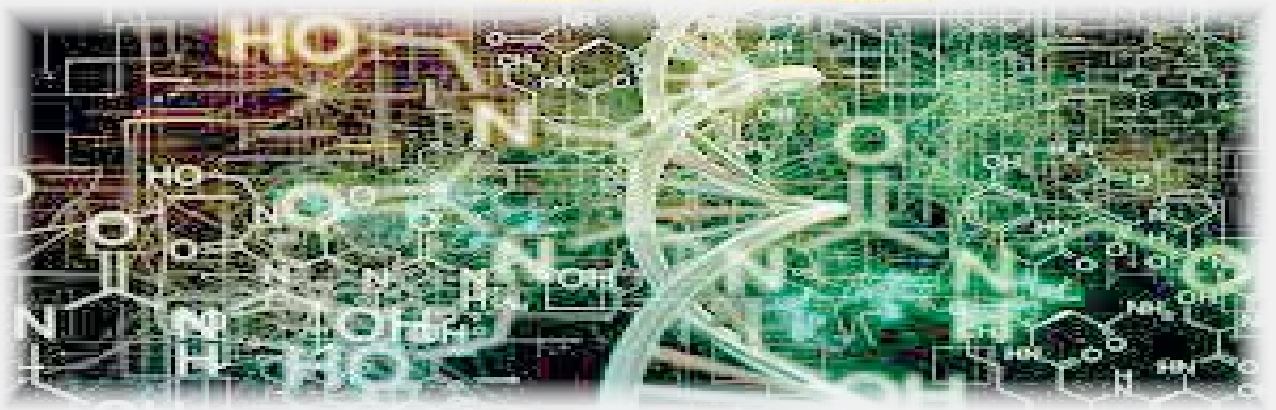


## Final revision on ch 8 ,1

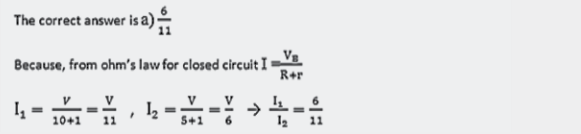
(1) In the figure, the ratio  $\frac{I_1}{I_2} = \dots$



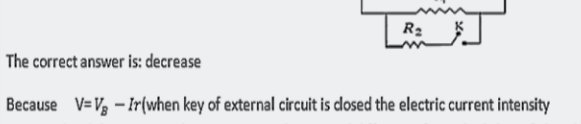
(2) In the circuit shown in the figure what happens to the voltmeter reading when the (K) is closed



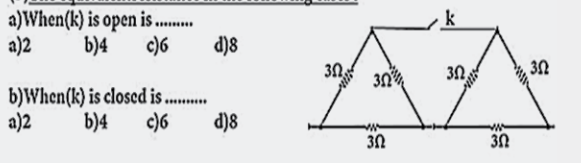
(3) The equivalent resistance in the following cases:



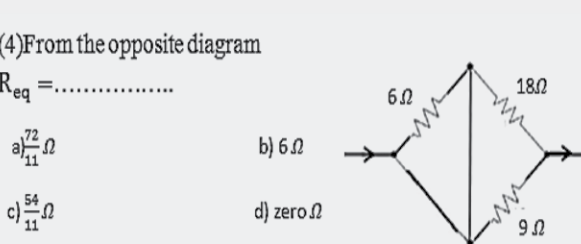(4) From the opposite diagram  $R_{eq} = \dots$



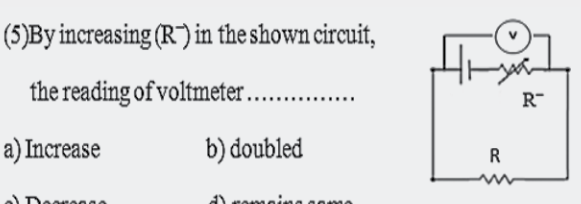(5) By increasing (R) in the shown circuit, the reading of voltmeter .....




The correct answer is : decreases


Because; if the battery has an internal resistance r  
The reading of voltmeter  $V = V_B - I(R + r)$

(6) If the length of a metal conductor is doubled, and its radius decrease to half, so the specific resistance is .....

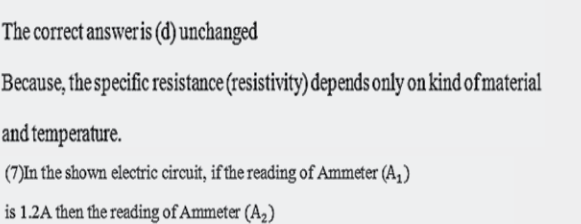
(7) In the shown electric circuit, if the reading of Ammeter ( $A_1$ ) is 1.2A then the reading of Ammeter ( $A_2$ ) is .....



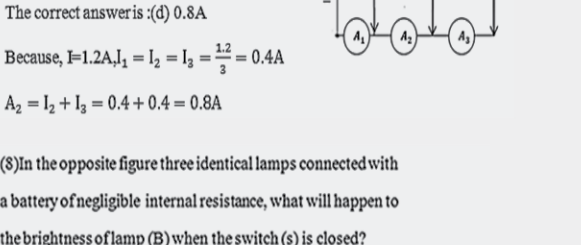
(8) In the opposite figure three identical lamps connected with a battery of negligible internal resistance, what will happen to the brightness of lamp (B) when the switch (S) is closed?



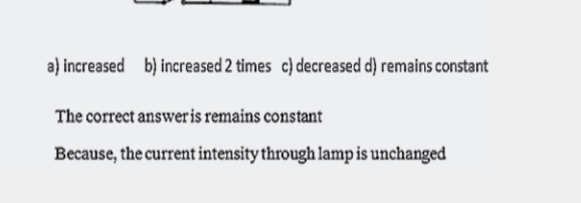
(9) In the circuit shown, the value of resistance (R) equals .....



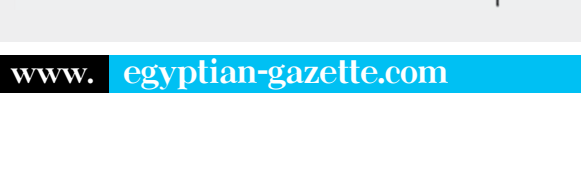
(10) In the opposite figure, if the current intensity passing through resistance  $2\Omega$  equals 1A, so the current through resistance  $12\Omega$  equals .....



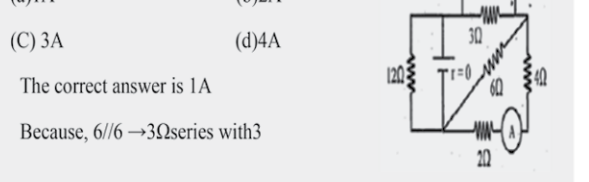
(11) From the opposite figure electric circuit, which of the following is the correct answer:



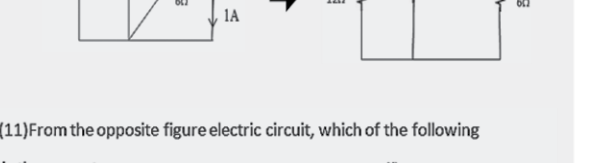(12) In the given circuit find the current intensities:  $I_1, I_2$  and  $I_3$



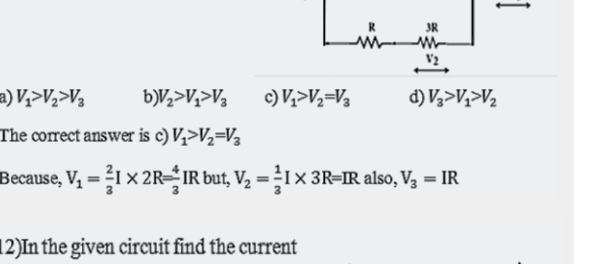(13) From the opposite electric circuit shown in figure, answer the following quest:



(14) In a pure Si crystal the concentration of each free electrons or holes is  $1.5 \times 10^{10} \text{ cm}^{-3}$  if it is doped with 5-valency Arsenic by the concentration  $10^{17} \text{ cm}^{-3}$  atoms  $\text{cm}^{-3}$ , then the concentration of both free electrons and holes in the doped crystals are .....

(15) If you know that the concentration of free electrons or holes in a pure Ge crystal is  $10^{15} \text{ cm}^{-3}$ . Antimony is added with concentration  $6 \times 10^{17} \text{ cm}^{-3}$  and also boron is added with concentration of  $10^{17} \text{ cm}^{-3}$ .


(16) The concentration of free electrons or holes in pure silicon is  $2.4 \times 10^{13} \text{ cm}^{-3}$ . If concentration of Si atoms is  $4.42 \times 10^{23}$  atoms  $\text{cm}^{-3}$  and silicon is doped with phosphorus in concentration of one phosphorus atom in one million Si atoms the concentration of free electrons and holes are .....

(17) A diode has a resistance  $200\Omega$  in forward bias connection.


(18) In a transistor the ratio between the collector current and emitter current is  $\alpha_e = 0.99$  and the base current has intensity  $50 \mu\text{A}$ .

(19) An npn transistor works as a switch with  $V_{CC} = 10 \text{ V}$  and  $R_C = 1000 \Omega$ , in the following cases

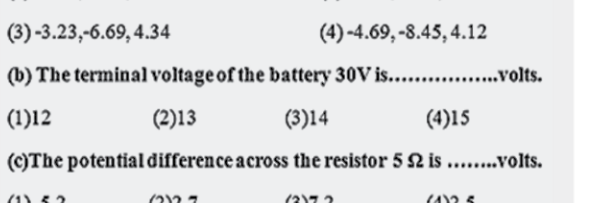
(20) The circuit represents a transistor as inverter gate, if the output Potential ( $V_{CE}$ ) = 0.8V when the resistance of the base circuit ( $R_B = 4000\Omega$ ), so the value of the collector circuit resistance ( $R_C$ ) = ... approximately.



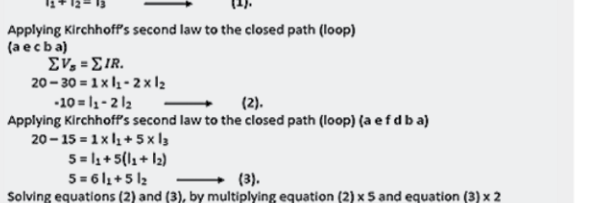
(21) The circuit represents a transistor as an amplifier, if the voltmeter reads 4.8V, and the value of  $R_C = 4.5\text{K}\Omega$  So, the values of  $\beta$ , and  $\alpha$ , respectively are .....



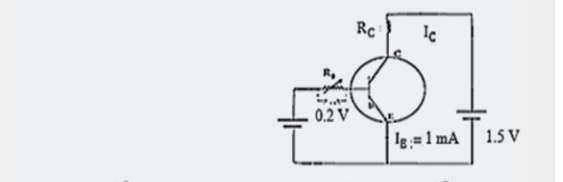(22) Calculate the potential difference between each of the following two points:



(23) From the opposite figure calculate:

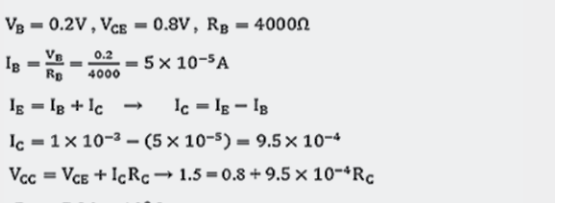


(24) A diode has a resistance  $200\Omega$  in forward bias connection.

(25) The current passing in it if a reverse bias of -4v is applied on it is .....


(26) In a transistor the ratio between the collector current and emitter current is  $\alpha_e = 0.99$  and the base current has intensity  $50 \mu\text{A}$ .

(27) An npn transistor works as a switch with  $V_{CC} = 10 \text{ V}$  and  $R_C = 1000 \Omega$ , in the following cases

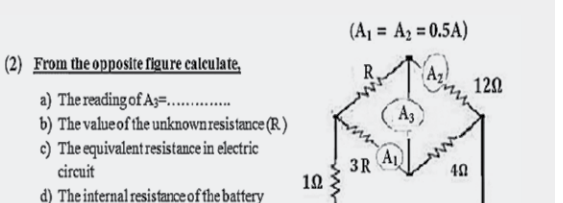
(28) The circuit represents a transistor as inverter gate, if the output Potential ( $V_{CE}$ ) = 0.8V when the resistance of the base circuit ( $R_B = 4000\Omega$ ), so the value of the collector circuit resistance ( $R_C$ ) = ... approximately.



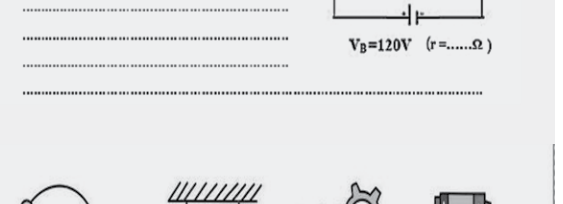(29) The circuit represents a transistor as an amplifier, if the voltmeter reads 4.8V, and the value of  $R_C = 4.5\text{K}\Omega$  So, the values of  $\beta$ , and  $\alpha$ , respectively are .....



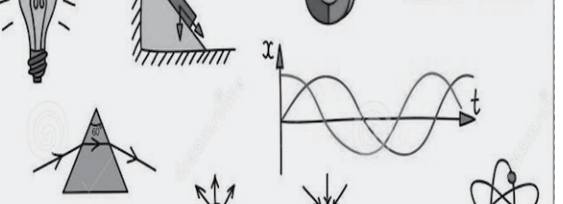(30) Calculate the potential difference between each of the following two points:



(31) From the opposite figure calculate:



(32) A diode has a resistance  $200\Omega$  in forward bias connection.

(33) In a transistor the ratio between the collector current and emitter current is  $\alpha_e = 0.99$  and the base current has intensity  $50 \mu\text{A}$ .